

# Differential Amplifier with $R_B$

H R Pota

April 12, 2007

## 1 Notation

In most electronic circuits both DC and small-signal voltages are applied simultaneously. The DC voltage is applied to set the bias and small-signals are the ones which are generally amplified or processed by electronic circuits. A little attention to notation helps immensely in the analysis of all electronic circuits.

$V_{BE}$  — DC voltage *only* of node  $B$  with respect to node  $E$  (all uppercase letters)

$v_{be}$  — small-signal voltage *only* of node  $B$  with respect to node  $E$  (all lowercase letters)

$v_{BE}$  — total voltage of node  $B$  with respect to node  $E$  ( $v$  lowercase, subscript uppercase)

Note that the total voltage  $v_{BE} = V_{BE} + v_{be}$ . When there is just one subscript, as compared to double in the preceding discussion, the uppercase-lowercase notation is the same but all the voltages are referred with respect to ground. The same notation is used for currents. In the following the total current  $i_C$  is the sum of the DC current  $I_C$  and small-signal current  $i_c$ .

$$i_C = I_C + i_c$$

## 2 Differential Amplifier with Base Resistance

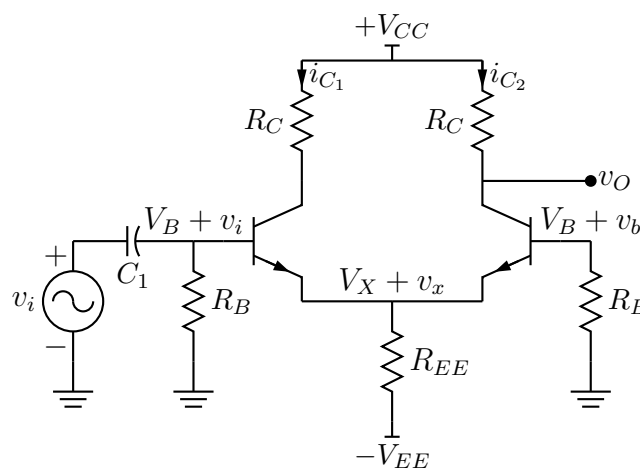


Figure 1: Differential Amplifier with  $R_{EE}$

The bias currents are (assuming that the transistors are identical):

$$I_C = I_{C1} = I_{C2} = I_S e^{(V_B - V_X)/V_T} = \frac{V_X + V_{EE}}{2R_{EE}}$$

### Equations to work out $v_x$ and $v_b$

We need two equations to work out  $v_x$  and  $v_b$ .

**The first equation** We first write the KCL at the node where  $R_{EE}$  and both the emitters meet,

$$I_S e^{(V_B + v_i - V_X - v_x)/V_T} + I_S e^{(V_B + v_b - V_X - v_x)/V_T} = 2I_C + \frac{v_x}{R_{EE}}. \quad (1)$$

Equation (1) can be rewritten as:

$$I_C e^{(v_i - v_x)/V_T} + I_C e^{(v_b - v_x)/V_T} = 2I_C + \frac{v_x}{R_{EE}} \quad (2)$$

$$I_C \left(1 + \frac{v_i - v_x}{V_T} + \dots\right) + I_C \left(1 + \frac{v_b - v_x}{V_T} + \dots\right) = 2I_C + \frac{v_x}{R_{EE}} \quad (3)$$

$$I_C \left(\frac{v_i - 2v_x + v_b}{V_T}\right) = \frac{v_x}{R_{EE}} \quad (4)$$

The step from equation (3) to equation (4) is valid when  $|v_i - v_x| \ll V_T$  and  $|v_b - v_x| \ll V_T$ .

**The second equation** Next we see that the collector and base currents in the right hand side transistor are related as:

$$I_S e^{(V_B + v_b - V_X - v_x)/V_T} = -\beta \frac{V_B + v_b}{R_B} \quad (5)$$

$$I_C e^{(v_b - v_x)/V_T} = -\beta \frac{V_B + v_b}{R_B} \quad (6)$$

$$I_C \left(1 + \frac{v_b - v_x}{V_T}\right) = -\beta \frac{V_B + v_b}{R_B} \quad (7)$$

Note that  $I_C = -\beta \frac{V_B}{R_B}$  and defining  $g_m = \frac{I_C}{V_T}$  we obtain from (7)

$$v_b = \frac{g_m R_B}{\beta + g_m R_B} v_x \quad (8)$$

**Putting them together** Substituting the above expression (8) of  $v_b$  in equation (4), we get

$$v_x = \frac{v_i}{2 - \frac{g_m R_B}{\beta + g_m R_B} + \frac{1}{g_m R_{EE}}} \quad (9)$$

For  $\beta \ll g_m R_B$  and  $R_{EE} \rightarrow \infty$ ,

$$v_b = v_x \text{ and } v_x = v_i$$

and when  $\beta \rightarrow \infty$  and  $R_{EE} \rightarrow \infty$ ,

$$v_b = 0 \text{ and } v_x = \frac{v_i}{2}.$$